EE5811: FPGA LAB

P V Aishwarya IS21MTECH14004 February 10, 2022

Problem

Question 5) c) from papers/icse/cs/2018.pdf Simplify the following expression using Boolean Laws :

$$A.(A' + B).C.(A + B)$$

Implement above program in Arduino.

Solution

Truth Table

A	B	C	LHS	RHS
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	0	0
1	0	0	0	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Table 1: Truth table for A.(A' + B).C.(A + B) = A.B.C

Implemented the above truth table in Arduino. The inputs A,B,C equivalent are displayed on seven segment display and its corresponding output is displayed with LED. Steps:

- 1. Wrote the program in termux (main.cpp)
- 2. Generated hex file (firmware.hex) for the program and sent the file to laptop.
- 3. On laptop used XLoader to load the hex file onto Arduino.